



VCO 5A

The VCO 5A is based on the National Semiconductor application notes for the LM13600/LM13700 dual ota. It is simple to build, low in cost ,easy to scale and stable. The output waveforms are terrific sounding and looking. It's almost too good to be true.

Thanks to Romeo for the tri to saw converter. I tried the 3080 tri to sine converter but I like the Format type better.

PCB is untested.


